

Assignment 4

Due: 8:00pm, Tuesday, March 24

Problem 5.14

5.14 Consider an n -channel MOSFET with $t_{ox} = 4$ nm, $\mu_n = 450$ cm²/V · s, $V_t = 0.5$ V, and $W/L = 10$. Find the drain current in the following cases:

- (a) $v_{GS} = 1.8$ V and $v_{DS} = 1$ V
- (b) $v_{GS} = 0.7$ V and $v_{DS} = 1.5$ V
- (c) $v_{GS} = 1.8$ V and $v_{DS} = 0.1$ V
- (d) $v_{GS} = v_{DS} = 1.8$ V

Problem 5.17

5.17 A particular MOSFET for which $V_m = 0.4$ V and $k'_n(W/L) = 2$ mA/V² is to be operated in the saturation region. If i_D is to be 50 μ A, find the required v_{GS} and the minimum required v_{DS} . Repeat for $i_D = 200$ μ A.

Problem 5.21

5.21 For an NMOS transistor, for which $V_t = 0.5$ V, operating with v_{GS} in the range of 1.0 V to 1.8 V, what is the largest value of v_{DS} for which the channel remains continuous?

Problem 5.44

5.44 The NMOS transistor in the circuit of Fig. P5.43 has $V_t = 0.4$ V and $k_n = 4$ mA/V². The voltages at the source and the drain are measured and found to be -0.55 V and $+0.1$ V, respectively. What current I_D is flowing, and what must the values of R_D and R_S be? What is the largest value for R_D for which I_D remains unchanged?

Problem 5.46

5.46 The transistor in the circuit of Fig. P5.46 has $k'_n = 0.5 \text{ mA/V}^2$, $V_t = 0.4 \text{ V}$, and $\lambda = 0$. Show that operation at the edge of saturation is obtained when the following condition is satisfied:

$$\left(\frac{W}{L}\right)R_D = 2.5 \text{ k}\Omega$$

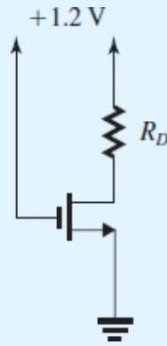


Figure P5.46

Problem 5.53

5.53 The MOSFET in Fig. P5.53 has $V_t = 0.4 \text{ V}$, $k'_n = 500 \mu\text{A/V}^2$, and $\lambda = 0$. Find the required values of W/L and R so that when $V_I = V_{DD} = +1.3 \text{ V}$, $r_{DS} = 50 \Omega$ and $V_O = 50 \text{ mV}$.

▼ Show Answer

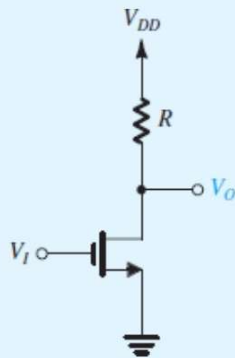


Figure P5.53