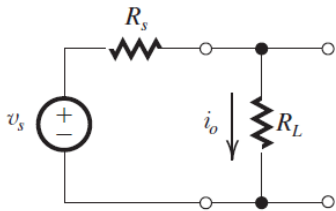


EMTR 1030 – Electronics

Assignment 1

Reference Solutions

Q1. Problem 1.26



$$\frac{i_o}{v_s} = \frac{1}{R_L + R_s}$$
$$\Rightarrow v_s = i_o (R_L + R_s)$$

Thus,

$$v_s = 10^{-4} \times (10^5 + R_s) = 10 + 10^{-4} \times R_s \quad (1)$$

and,

$$v_s = 5 \times 10^{-4} (10^4 + R_s) = 5 + 5 \times 10^{-4} \times R_s \quad (2)$$

Subtracting equation (2) from equation (1) gives

$$0 = 5 - 4 \times 10^{-4} \times R_s$$

$$\Rightarrow R_s = \frac{5}{4 \times 10^{-4}} = 12.5 \text{ k}\Omega$$


Substituting into equation (1),

$$v_s = 10 + 10^{-4} \times 12.5 \times 10^3 = 11.25 \text{ V}$$

Finally, the Norton equivalent source is found as follows,

$$i_s = v_s / R_s = 900 \mu\text{A}$$

Q2. Problem 1.46

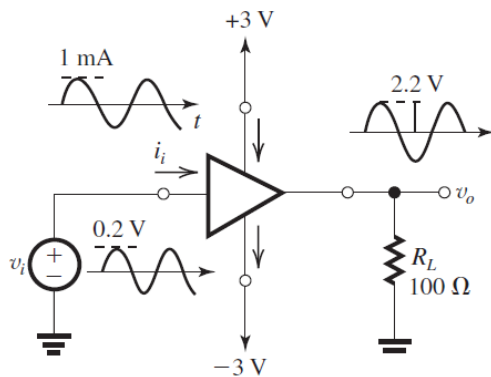

The voltage gain is

$$\frac{V_o}{V_i} = \frac{2.2}{0.2} = 11 \text{ V/V} = 20.8 \text{ dB}$$

The current gain is

$$\frac{I_o}{I_i} = \frac{2.2/0.1}{1.0} = 22 \text{ A/A} = 26.8 \text{ dB}$$

The power gain is

$$\frac{V_o I_o / 2}{V_i I_i / 2} = 11 \times 22 = 242 \text{ W/W} = 23.8 \text{ dB}$$

The supply power is

$$\frac{V_o^2}{2R_L} \times \frac{1}{\eta} = \frac{2.2^2}{2 \times 0.1 \times 0.1} = 242 \text{ mW}$$


Since the power is drawn from $\pm 3 \text{ V}$ supplies, the supply current must be

$$\frac{242}{3 - (-3)} = 40.3 \text{ mA}$$

The power dissipated in the amplifier is the total power drawn from the supply, less the power dissipated in the load.

$$242 - \frac{2.2^2}{2 \times 0.1} = 217.8 \text{ mW}$$

Q3. Problem 2.3

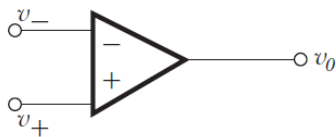

$$v_o = -3.500 \text{ V}$$

$$v_- = -1.000 \text{ V}$$

For ideal op amp,

$$v_+ = v_- = -1.000 \text{ V}$$

Measured voltage at positive input = -1.002 V

$$\text{Amplifier gain } A = \frac{v_o}{v_+ - v_-}$$

$$= \frac{-3.500}{-1.002 - (-1.000)}$$

$$= 1750 \text{ V/V}$$

Q4. Problem 2.10


Closed-loop gain is

$$\frac{v_O}{v_I} = -\frac{R_2}{R_1} = -\frac{10 \text{ k}\Omega}{10 \text{ k}\Omega}$$
$$= -1 \text{ V/V}$$

For $v_I = +1.00 \text{ V}$,

$$v_O = -1 \times 1.00$$

$$= -1.00 \text{ V}$$

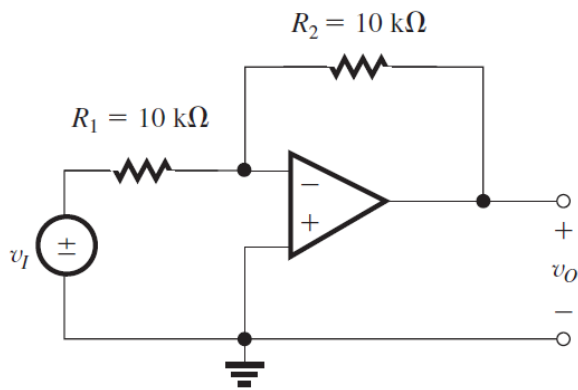


The two resistors are 1% resistors

$$\left| \frac{v_O}{v_I} \right|_{\min} = \frac{10(1 - 0.01)}{10(1 + 0.01)} = 0.98 \text{ V/V}$$

$$\left| \frac{v_O}{v_I} \right|_{\max} = \frac{10(1 + 0.01)}{10(1 - 0.01)} = 1.02 \text{ V/V}$$

Thus the measured output voltage will range from -0.98 V to -1.02 V .

Q5. Problem 2.45

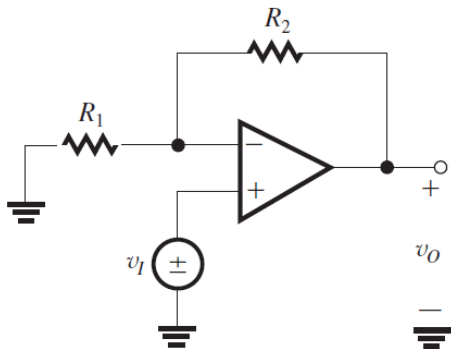

$$\frac{v_O}{v_I} = 1 + \frac{R_2}{R_1}$$

$$(a) \frac{v_O}{v_I} = 5 = 1 + \frac{R_2}{R_1}$$

$$\frac{R_2}{R_1} = 4; \text{ set } R_1 = 10 \text{ k}\Omega, R_2 = 40 \text{ k}\Omega$$

$$(b) \frac{v_O}{v_I} = 10 = 1 + \frac{R_2}{R_1}$$

$$\frac{R_2}{R_1} = 9; \text{ set } R_1 = 10 \text{ k}\Omega, R_2 = 90 \text{ k}\Omega$$

$$(c) \frac{v_O}{v_I} = 21 = 1 + \frac{R_2}{R_1}$$

$$\frac{R_2}{R_1} = 20; \text{ set } R_1 = 10 \text{ k}\Omega, R_2 = 200 \text{ k}\Omega$$


$$(d) \frac{v_O}{v_I} = 100 = 1 + \frac{R_2}{R_1}$$

$$\frac{R_2}{R_1} = 99; \text{ set } R_1 = 10 \text{ k}\Omega, R_2 = 990 \text{ k}\Omega$$

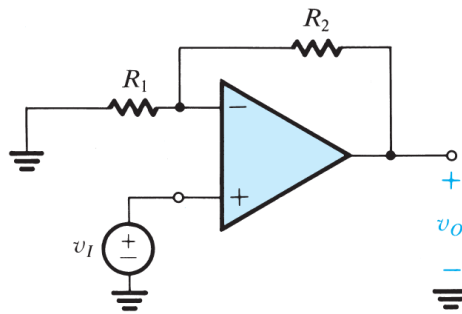Q6:


Consider the noninverting amplifier as shown in the following graph, with $R_1 = 2 \text{ k}\Omega$ and $R_2 = 10 \text{ k}\Omega$, and an ideal closed-loop gain of 100.

- Find the closed-loop gain if $A = 10^5$. Determine the percentage error in the magnitude of G relative to the ideal value of $1 + R_2/R_1$. Also determine the voltage v_1 that appears at the noninverting input terminal when $v_I = 0.2 \text{ V}$.
- If the open-loop gain A changes from 10^5 to 10^4 , what is the corresponding percentage change in the magnitude of the closed-loop gain G ?



Reference Solution

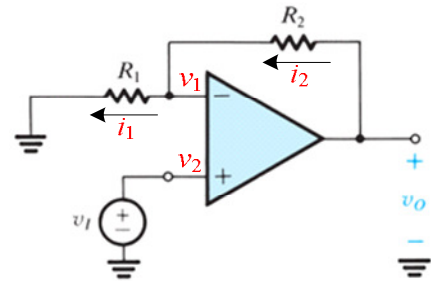- (a) There are two typos: the ideal gain of a non-inverting Op-amp should be $1 + \frac{R_2}{R_1}$, instead of $\frac{R_2}{R_1}$. Given $R_1 = 2 \text{ k}\Omega$ and $R_2 = 10 \text{ k}\Omega$, the ideal gain should be 6, instead of 100.



$$\text{The ideal gain: } G = \frac{v_o}{v_I} = 1 + \frac{R_2}{R_1} = 1 + \frac{10}{2} = 6$$

If $A = 10^5$, the real gain will be

$$G' = \frac{v_o}{v_I} = \frac{1 + R_2/R_1}{1 + (1 + R_2/R_1)/A} = 5.9996$$

$$\text{Percentage gain change: } \frac{G' - G}{G} = \frac{5.9996 - 6}{6} = -6.67 \times 10^{-5} = -0.00667\%$$

$$v_I = v_2, v_1 = v_2 = 0.2V$$

- (b) If the gain $A = 10^4$, the real gain will be

$$G' = \frac{v_o}{v_I} = \frac{1 + R_2/R_1}{1 + (1 + R_2/R_1)/A} = 5.9964.$$

In comparison with the real gain of 5.9996 when the gain $A = 10^5$, the change is:

$$\frac{5.9996 - 5.9964}{5.9996} = 5.334 \times 10^{-4} = 0.005334\%$$

Or even though A has a 10 times change, the real close-loop gain change is negligible!