

EMTR-2011: Microcontrollers and Digital Logic
Assignment 1

Due date: 1:00PM, Wednesday, Sept 25

Question 1

Do the following conversions:

- (1) 11101101_2 to decimal.
- (2) 101011010111 to hex.
- (3) $32BH$ to binary.
- (4) The following hexadecimal numbers to decimal.
 - (a) $6B2H$;
 - (b) $9F2EH$
- (5) The following decimal numbers to hex:
 - (a) 75 ;
 - (b) 938 ;
 - (c) 2048

Question 2

Use 2's complement method to do the following subtractions:

- (a) $11011 - 10101$
- (b) $110010 - 111001$

Question 3

Verify the following functions

- (a) $\overline{x \cdot y} = \bar{x} + \bar{y}$ (De Morgan's law)
- (b) $x \cdot y + y \cdot z + \bar{x} \cdot z = x \cdot y + \bar{x} \cdot z$ (Consensus)

Question 4

- (a) Design a logic circuit with two inputs, x_1 and x_2 , with required behavior shown in the truth table.

x_1	x_2	f
0	0	1
0	1	0
1	0	1
1	1	1

- (b) Use the Karnaugh map to derive the circuit output.

Question 5

Construction the Karnaugh maps based on the following truth tables and derive the circuit outputs.

(a)

x_1	x_2	x_3	f
0	0	0	1
0	0	1	0
0	1	0	1
0	1	1	0
1	0	0	1
1	0	1	1
1	1	0	1
1	1	1	0

(b)

x_1	x_2	x_3	f
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	1